

Digital Logic Circuits
'Memory Elements'
ELEC2200
Summer 2009

David J. Broderick
brodedj@auburn.edu
<http://www.auburn.edu/~brodedj>
Office: Broun 360




Memory Elements

- Combinational Logic
 - Output is function of inputs only
- Sequential Logic
 - Output is function of inputs **and** previous outputs
- We need a way to `remember' a previous logical value
- 2 basic types of memory elements
 - Latches – Level-sensitive to inputs
 - Flip-flops – Edge triggered on active edge of clock



Set-Reset Latch (NOR)

 
- Simplest Memory Element
- 2 NOR gates with feedback
 - Level sensitive
 - Active High
 - Input must be high to perform command
 - Only one input can be active
- Outputs: current state and its inverse



Set-Reset Latch (NOR)

- Recall the NOR gate:

X	Y	$(X+Y)'$
0	0	1
0	1	0
1	0	0
1	1	0

 


- This leads to:

R	S	Q^*	Q'	Command
0	0	Q	Q'	Remember
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Invalid




Set-Reset Latch (NOR)

R	S	Q*	Q'	Command
0	0	Q	Q'	Remember
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Invalid

 

- Timing Diagram

 


Set-Reset Latch (NOR)

- State Diagram

- In this case:

- State is output(Q)
- Each transition has a stimulus, (SR)

 - Don't cares still used for some stimuli



R	S	Q*	Q'*	Command
0	0	Q	Q'	Remember
0	1	1	0	Set
1	0	0	1	Reset
1	1	?	?	Invalid

$$Q^* = S + \bar{R}Q$$



Characteristic Equation

- Output of sequential logic is not only dependent on inputs but also the previous states
- $Q^* = f(S, R, Q)$
- For an SR Latch:


Q \ RS	00	01	11	10	R	S	Q*	Q'*	Command
0	0	1	X	0	0	0	Q	Q'	Remember
1	1	1	X	0	0	1	1	0	Set
					1	0	0	1	Reset
					1	1	?	?	Invalid

$Q^* = S + \bar{R}Q$



Set-Reset Latch (NAND)

 - Dual circuit
- 2 NAND gates with feedback
 - Level sensitive
 - Active **Low**
 - Input must be **low** to perform command
 - Only one input can be active
- Outputs: current state and its inverse
- Outputs reversed from NOR SR latch




Set-Reset Latch (NAND)

- Recall the NAND gate:

X	Y	$(X \cdot Y)'$
0	0	1
0	1	1
1	0	1
1	1	0


- This leads to:

R	S	Q^*	Q'^*	Command
0	0	Q	Q'	Invalid
0	1	1	0	Reset
1	0	0	1	Set
1	1	?	?	Storage

 

Gated SR Latch

 - If new input, E (enable), is inactive (low in this case) latch will be in 'remember' state
- Still level sensitive, so still a latch
- Active high inputs
 - E (enable)
 - R (Reset)
 - S (Set)
- Invalid command still possible
- Dual circuit also possible (NAND)




E	R	S	Q*	Q'*	Command
0	x	x	Q	Q'	Remember
1	0	0	Q	Q'	Remember
1	0	1	1	0	Set
1	1	0	0	1	Reset
1	1	1	?	?	Invalid




Gated SR Latch

E	R	S	Q*	Q'*	Command
0	x	x	Q	Q'	Remember
1	0	0	Q	Q'	Remember
1	0	1	1	0	Set
1	1	0	0	1	Reset
1	1	1	?	?	Invalid

 


- Timing Diagram

 

Gated SR Latch

 - State Diagram
- Don't cares on inputs can be 0 or 1
- If $E=0$, other inputs don't matter
- When $Q=0$, both reset and remember will remain in the same state
- When $Q=1$, both set and remember will remain in the same state



ERS

E	R	S	Q^*	Q'^*	Command
0	x	x	Q	Q'	Remember
1	0	0	Q	Q'	Remember
1	0	1	1	0	Set
1	1	0	0	1	Reset
1	1	1	?	?	Invalid



Characteristic Equation

- Gated SR Latch

QE \ RS	00	01	11	10	E	R	S	Q*	Q'*	Command
00	0	0	0	0	0	x	x	Q	Q'	Remember
01	0	1	x	0	1	0	0	Q	Q'	Remember
11	1	1	x	0	1	0	1	1	0	Set
10	1	1	1	1	1	1	0	0	1	Reset
					1	1	1	?	?	Invalid

$$Q^* = SE + QR + \bar{E}Q$$





Enabled Data Latch

- AKA: Delay Latch, D Latch, transparent D Latch
- No more undefined state!


E	D	Q*	Command
0	x	Q	Remember
1	0	0	Transparent
1	1	1	Transparent

  - When enabled (E=1) the latch is transparent (Q=D)




Enabled Data Latch

E	D	Q*	Command
0	x	Q	Remember
1	0	0	Transparent
1	1	1	Transparent

 


Timing Diagram

 

Enabled Data Latch

 - D Latch State Diagram
 - Still only two states,
 - Stimulus changed
- When $Q=0$, both reset and remember will remain in the same state
- When $Q=1$, both set and remember will remain in the same state



E	D	Q*	Command
0	x	Q	Remember
1	0	0	Transparent
1	1	1	Transparent



Characteristic Equation

- Enabled D Latch


Q\ED		ED				Q*	Command
		00	01	11	10		
0	0	0	0	1	0	Q	Remember
	1	0	0	1	0	0	Transparent
1	0	1	1	1	1	1	Transparent
	1	1	1	0	1	1	Transparent

$$Q^* = DE + \overline{E}Q$$



Something to avoid

 - Transitions on D and E at the same time
- Inputs don't change instantaneously, can lead to unknown state




Flip-Flops

- Latches are level sensitive, transition when a level (0 or 1) is present on the inputs
- Flip-flops transition on a clock signal
 - Positive pulse
 - Negative pulse
 - Positive edge
 - Negative edge
- Can be built from basic gates or from latches




Master-Slave Flip-Flops

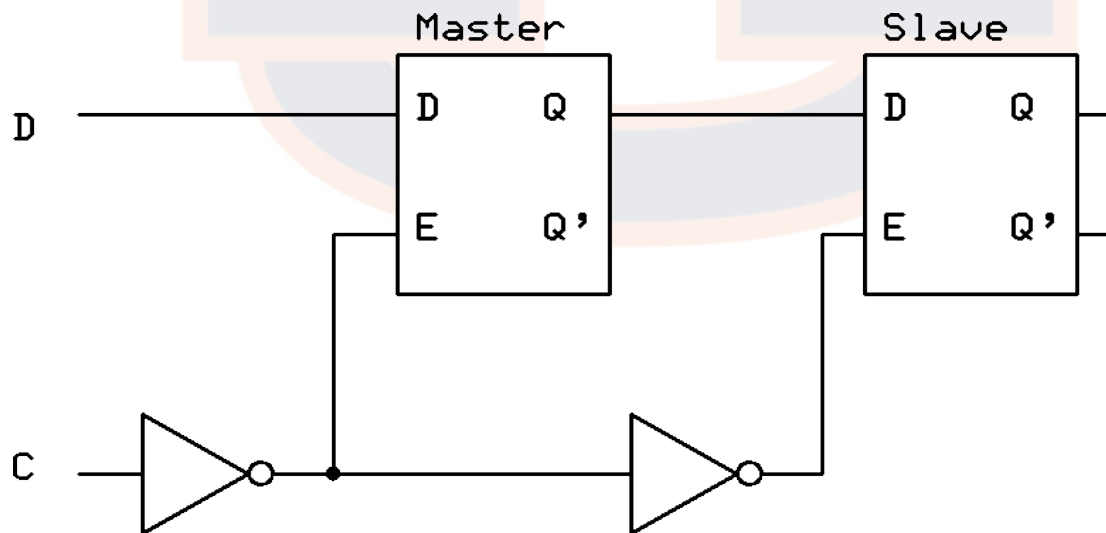- When clock is low
 - Master D latch is transparent
 - Slave D latch is remembering
- When clock is high
 - Master D latch is remembering
 - Slave D latch is transparent




Master-Slave Flip-Flops

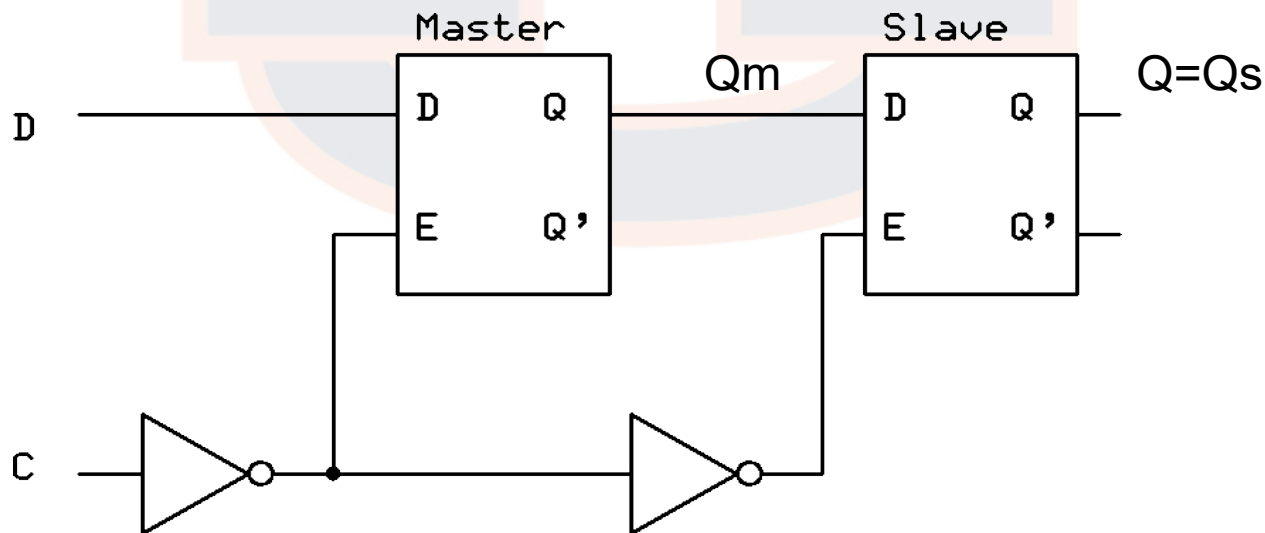
- Q_m can transition whenever C is low
- Q (Q_s) transitions on the positive edge of a pulse
- Whatever value was present on D when the positive edge of the clock (C) occurred is allowed to pass to Q at that time
- Ideally all transitions occur simultaneously




Master-Slave Flip-Flops

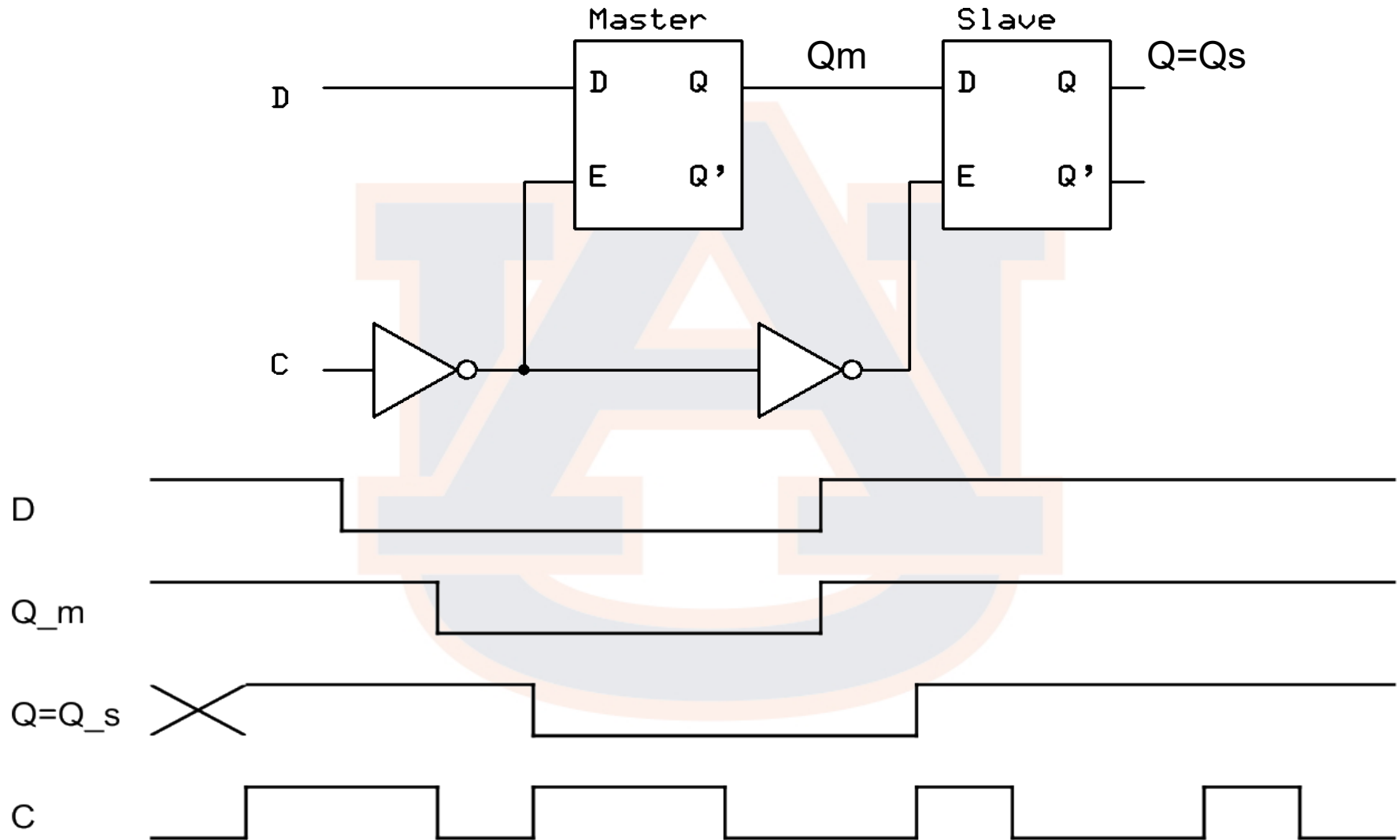

Master-Slave Flip-Flops

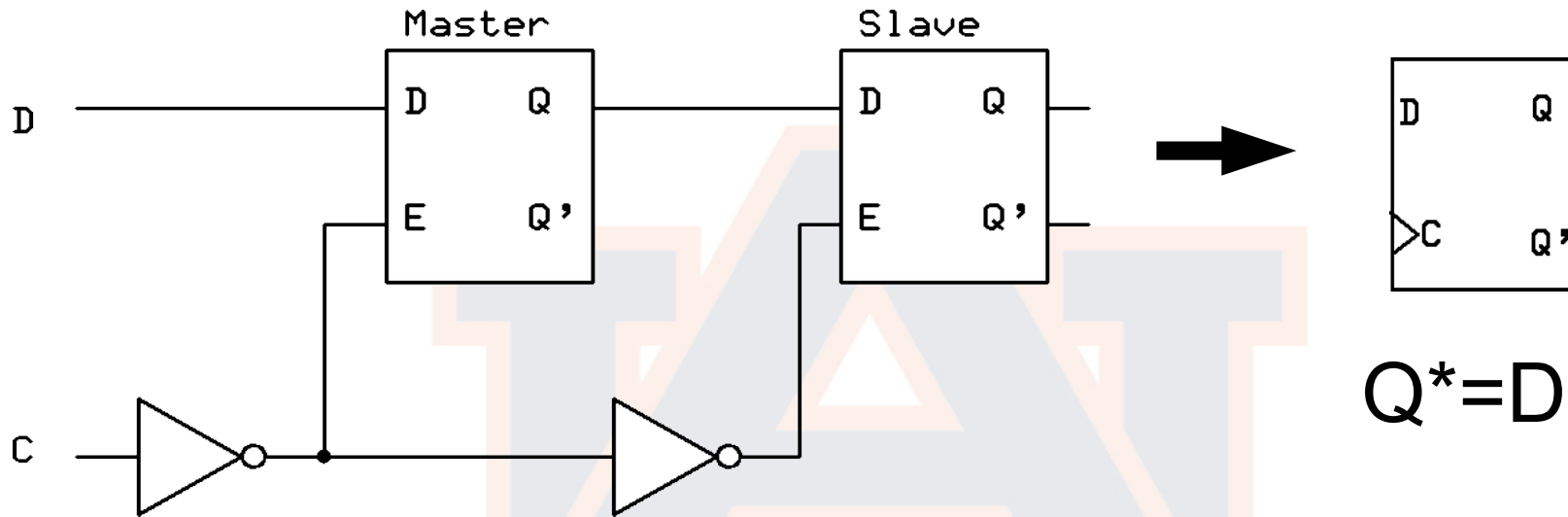


D	C	Q*	Command
0	↑	0	Reset
1	↑	1	Set

 


Master-Slave Flip-Flops

 - Negative edge of clock can be active too
- Q transitions on negative going edge of clock
- Negative edge is now the active edge



D	C	Q*	Command
0	↓	0	Reset
1	↓	1	Set

 

Characteristic Equation

- Master-Slave D Flip-flop

Q\D	0	1	D	C	Q*	Command
0	0	1	0	↓	0	Reset
1	0	1	1	↓	1	Set



$$Q^* = D$$



J-K Flip-Flop

- Another method of removing the invalid input present in a SR latch/flip-flop

J	K	C	Q*	Command
0	0	↑	Q	Remember
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	Q'	Toggle

  

Characteristic Equation

- JK Flip-flop

Q\JK	00	01	11	10	J	K	C	Q*	Command
0	0	0	1	1	0	0	↑	Q	Remember
1	1	0	0	1	0	1	↑	0	Reset
					1	0	↑	1	Set
					1	1	↑	Q'	Toggle



$$Q^* = \bar{K}Q + J\bar{Q}$$



Toggle (T) Flip-Flop

- Built from J-K Flip-flops
- Edge-triggered (1st type)

T	Q*	Command
↓	Q'	Toggle

  

Characteristic Equation

- T Flip-flop (edge triggered)

Q		T	Q*	Command
0	1	↓	Q'	Toggle
1	0			



$$Q^* = \overline{Q}$$



Toggle (T) Flip-Flop

- Built from J-K Flip-flops
- Clocked (2nd type)

T	C	Q*	Command
0	↓	Q	Remember
1	↓	Q'	Toggle

  

Characteristic Equation

- T Flip-flop (clocked)


Q\T	0	1	T	C	Q*	Command
0	0	1	0	↓	Q	Remember
1	1	0	1	↓	Q	Toggle

$$Q^* = \bar{T}Q + T\bar{Q}$$




Timing Considerations

 - Transitions don't actually happen simultaneously
- Minimum setup time (t_{su}) – minimum time D must be valid at input before active edge of clock
- Minimum hold time (t_h) – minimum time D must remain valid after active edge of clock
- Clock-to-output delay (t_{co}) – maximum time before Q is valid after the active edge of clock




Timing Considerations

 - Violations of these times must be avoided in design process
- If violation occurs:
 - Real circuit will resolve to an unknown state ($Q=Q'$)
 - Simulation will not be valid and can lead to invalid simulation and manufacturing problems (clock-data-races)



Clock Signals

 - Typically a periodic signal (a sequence of pulses) used to:
 - Sample data
 - Store sampled data in memory elements
- T = period of periodic signal, the time it take the signal to repeat itself
- f = clock frequency, $1/T$



Flip-Flop Initialization

- Some flip-flops have another set of inputs for initialization
- These input can be
 - Synchronous – Change output on active clock edge
 - Asynchronous – Change inputs regardless of active clock edge
- Initialization important:
 - To remove undefined logic value in simulation
 - Start a system in a known state



Flip-Flop Initialization

- Initialization inputs called:
 - Preset (pre) sets output (Q) to logic 1 (high)
 - Clear (clr) sets output (Q) to logic 0 (low)
- Initialization inputs can also be:
 - Active high – affect output when logic 1
 - Active low - affect output when logic 0



Flip-Flop Initialization

- For this example:
 - Preset (Pre) is active high and synchronous
 - Clear (Clr) is active low and asynchronous

